
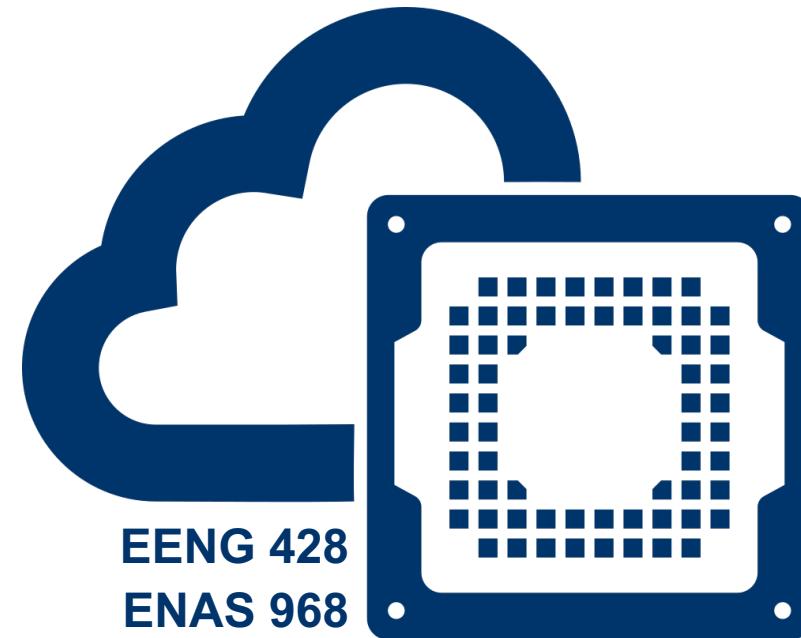


Cloud FPGA

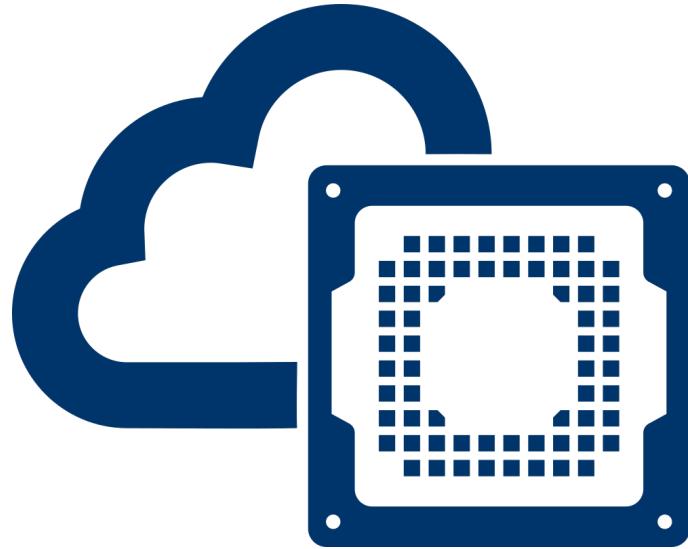

bit.ly/cloudfpga



Lecture: Logic Level Modeling

Prof. Jakub Szefer
Dept. of Electrical Engineering, Yale University


EENG 428 / ENAS 968
Cloud FPGA



Share:
bit.ly/cloudfpga

EENG 428 / ENAS 968 – Cloud FPGA
© Jakub Szefer, Fall 2019


Logic Synthesis

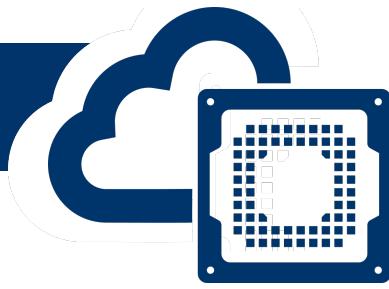

This lecture is mostly based on contents of Chapter 6, from “The Verilog Hardware Description Language” book [1], 5th edition. Example figures and (modified) code are from the textbook unless otherwise specified.


Topics covered:

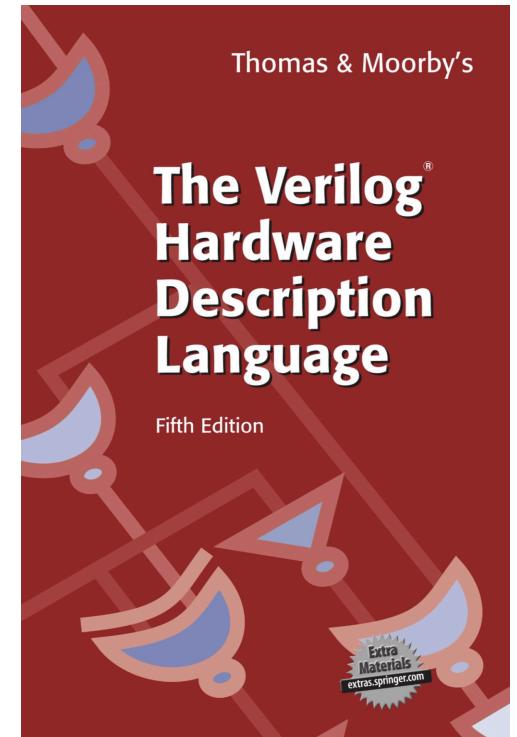- Logic gates and nets
- Four logic level values
- Continuous assignment
- Logic delay modeling
- Specifying time units



Share:
bit.ly/cloudfpga


Logic Level Modeling

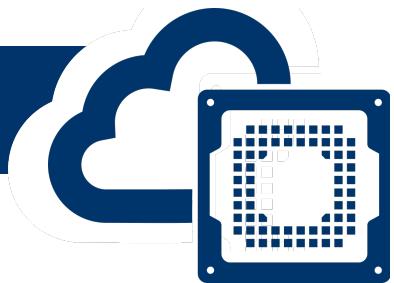

Share:
bit.ly/cloudfpga

EENG 428 / ENAS 968 – Cloud FPGA
© Jakub Szefer, Fall 2019

Logic Level Modeling

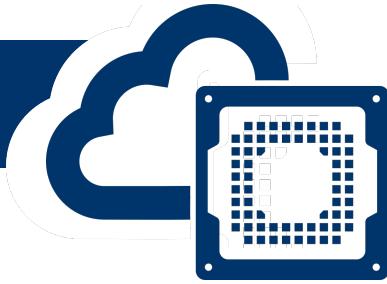

- Behavioral modeling focuses on describing behavior and functionality of a circuit
 - Behavioral code is written almost as a software-like function
- **Logic level modeling is used to model the logical structure of a design**
 - Specify ports (inputs and outputs)
 - Any submodule instances
 - Connection between the submodules
 - Logical functions
- Levels of logic modeling
 - 1) Gate level – describe design in terms of interconnection of logical gates
 - Use gate-level primitives
 - 2) Continuous assignment statements – describe designs using Boolean algebra-like expressions
 - Use `assign` statements
 - 3) Transistor switch level – describe at level of MOS and CMOS transistors

Note at the gate level, the actual implementation in FPGA will not use exactly the gates used in Verilog – all code is compiled to use Look-Up Tables (LUTs) in the FPGAs

FPGA and ASIC vendors provide modules such as LUT, DFF, etc. to let users exactly specify the hardware that will be implemented

Logic Gates and Nets



- Describing and modeling design at the logic level can be done using Verilog's built-in logic gate and switch primitives:


n_input gates	n_output gates	tristate gates	pull gates	MOS switches	bidirectional switches
and	buf	bufif0	pullup	nmos	tran
nand	not	bufif1	pulldown	pmos	tranif0
nor		notif0		cmos	tranif1
or		notif1		rnmos	rtran
xor				rpmos	rtranif0
xnor				rcmos	rtranif1

Used for logic-level modeling


Used for transistor-level modeling

- The gates (and switch level primitives) can be interconnected using **nets**
 - A **net** is a Verilog type, pretty much a representation of a physical wire
 - nets** do not store values or charges, except a **tirreg** type of a **net**

Logic Gates and Nets

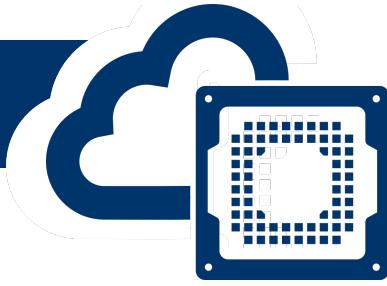

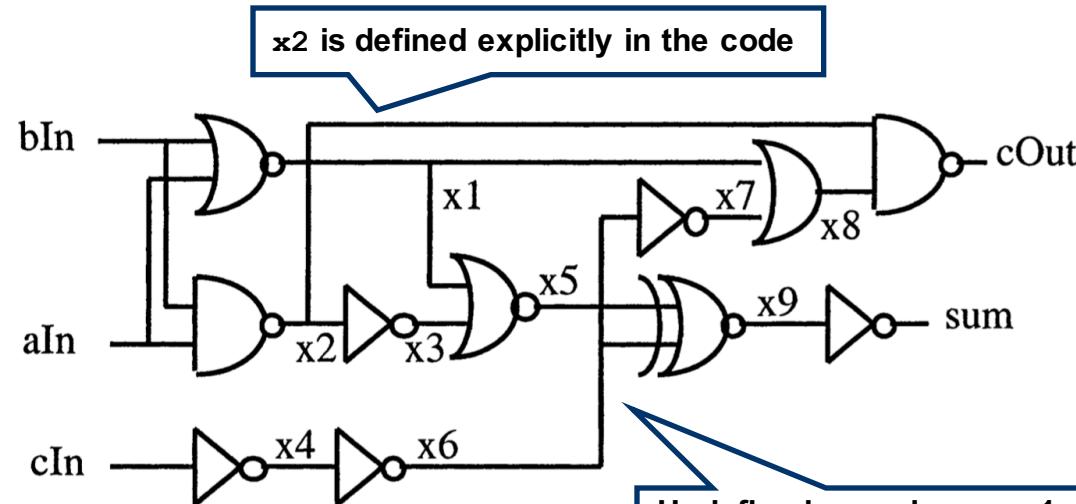- Textbook example of full adder module
 - Each gate is interconnected using **nets**
 - Inputs and outputs are wire **nets** by default
 - Undefined **nets** will be made into wires by default



Common problem is undefined wires that become 1-bit wires by default and cause logic to work incorrectly!

Can use ``default_netttype none` to disable automatic definition of wire nets

```
module fullAdder
( output c0ut, sum,
  input aIn, bIn, cIn
);

wire x2;

nand (x2, aIn, bIn),
      (c0ut, x2, x8);

xnor (x9, x5, x6);


nor (x5, x1, x3),
     (x1, aIn, bIn);

or (x8, x1, x7);

not (sum, x9),
     (x3, x2),
     (x6, x4),
     (x4, cIn),
     (x7, x6);

endmodule
```

Logic Gate Instance Options

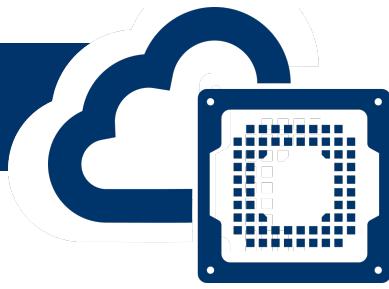

Gates (and modules, see later slides) can be instantiated with a number of options

- **Instance names** – are used in hierarchical design, a good practice is to assign meaningful and unique instance names to all modules and gates
- **Gate delay** – is used to quantify the number of time units form when any input changes to when output changes, this is the propagation delay
- **Drive (and charge) strength** – used for modeling physical behavior of wires
 - The drive strengths are: **supply**, **strong**, **pull**, **weak**, and **highz** (all **nets** except **trireg**)
 - The charge strengths are: **large**, **medium** and **small** strengths (for **trireg** only)
 - Higher drive strength can supply the needed current faster when switching

Strength and delay are not used
for writing code synthesized to
FPGAs (and ASICs)

```
nand (strong0, strong1) #3
  GateA (x2, aIn, bIn),
  GateB (cOut, x2, x8);
```



Share:
bit.ly/cloudfpga

Four Logic Level Values



- The values that may be driven onto a net are:
 - 0** – a logic zero, or FALSE condition
 - 1** – a logic one, or TRUE condition
 - x** – an unknown logic value (any of 0, 1, or in a state of change)
 - z** – a high-impedance condition
- Gate truth tables with respect to the possible logic levels (see textbook's Appendix D):

AND	0	1	x	z
0	0	0	0	0
1	0	1	x	x
x	0	x	x	x
z	0	x	x	x

NOT	output
0	1
1	0
x	x
z	x


Bufif0	Control Input			
	0	1	x	z
D	0	0	z	L
A	1	1	z	H
T	x	x	z	x
A	z	x	z	x

L indicates 0 or z; H indicates 1 or z



Share:
bit.ly/cloudfpga

Different net types

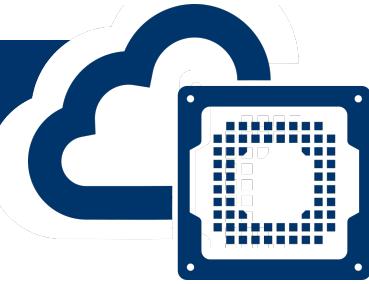

- **nets** are used to model electrical connections
 - **nets** store no charges and are just a connection
 - Except **trireg** that models wires as capacitors that store charge
- Many net types are supported in Verilog:
 - **wire, tri, tri1, supply0, wand, triand, tri0, supply1, wor, and trior**

Main type used for any
synthesizable code

Net Type	Modeling Usage
wire and tri	Used to model connections with no logic function. Only difference is in the name. Use appropriate name for readability.
wand, wor, triand, trior	Used to model the wired logic functions. Only difference between wire and tri version of the same logic function is in the name.
tri0, tri1	Used to model connections with a resistive pull to the given supply
supply0, supply1	Used to model the connection to a power supply
trireg	Used to model charge storage on a net. See Chapter 10.



Share:
bit.ly/cloudfpga


Logic Level Modeling Example



- Textbook of Hamming encoder and decoder and a simple testbench
 - Hamming codes can be used to detect and correct errors in transmitted data
 - Example uses code that can correct 1 error



Original Data	Encoding Function	Encoded Data
D1	$H1 = \text{XOR } (D1, D2, D4, D5, D7)$	encoded[1]
D2	$H2 = \text{XOR } (D1, D3, D4, D6, D7)$	encoded[2]
D3	$H4 = \text{XOR } (D2, D3, D4, D8)$	encoded[3]
D4	$H8 = \text{XOR } (D5, D6, D7, D8)$	encoded[4]
D5		encoded[5]
D6		encoded[6]
D7		encoded[7]
D8		encoded[8]
		encoded[9]
		encoded[10]
		encoded[11]
		encoded[12]

- Example test module:

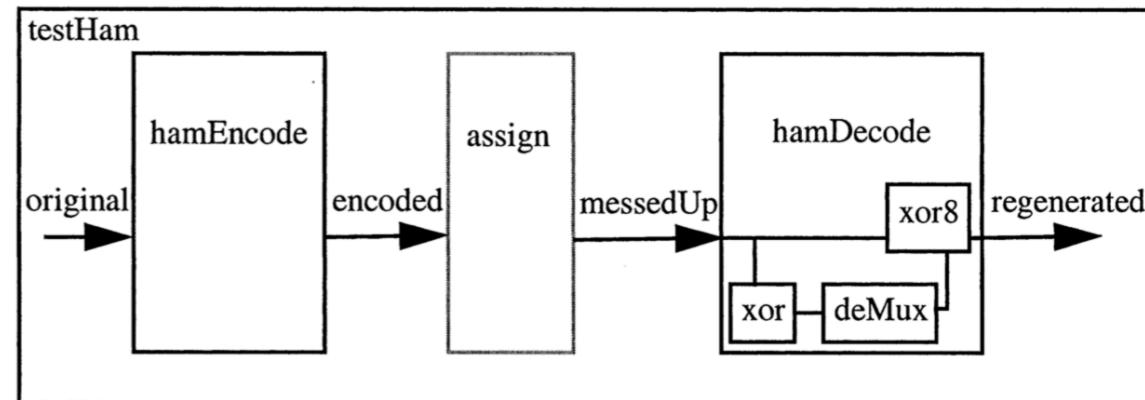

Share:
bit.ly/cloudfpga

Logic Level Modeling Example

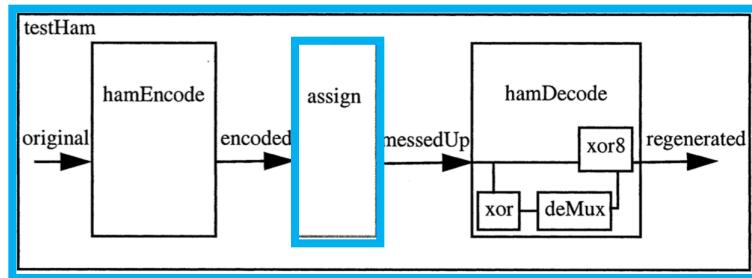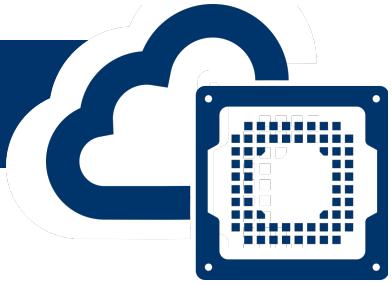

```
module testHam;

    reg [1:8] original;
    wire [1:8] regenerated;
    wire [1:12] encoded, messedException;

    integer seed;
    initial
    begin

        seed = 1;

        forever
        begin
            original = $random (seed);
            #1
            $display ("original=%h, encoded=%h, messedException=%h",
                      original, encoded, messedException, regenerated);
        end
    end

    hamEncode hIn (original, encoded);

    hamDecode h0out (messedException, regenerated);



    assign messedException = encoded ^ 12'b 0000_0010_0000;

endmodule
```



Share:
bit.ly/cloudfpga

Logic Level Modeling Example

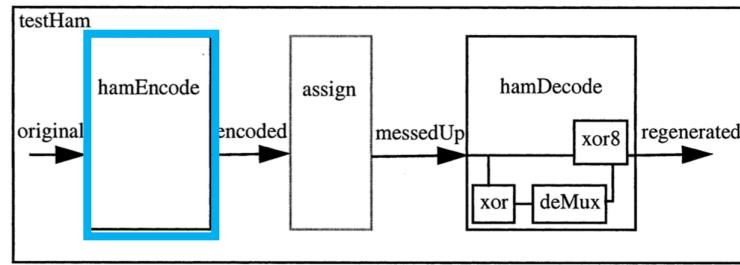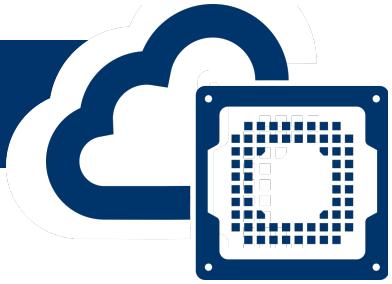

```
module hamEncode
( input [1:8] vIn,
  output [1:12] valueOut
);

  wire h1, h2, h4, h8;
  xor (h1, vIn[1], vIn[2], vIn[4], vIn[5], vIn[7]),
        (h2, vIn[1], vIn[3], vIn[4], vIn[6], vIn[7]),
        (h4, vIn[2], vIn[3], vIn[4], vIn[8]),
        (h8, vIn[5], vIn[6], vIn[7], vIn[8]);


  assign valueOut = {h1, h2, vIn[1], h4, vIn[2:4], h8, vIn[5:8]};

endmodule
```



Share:
bit.ly/cloudfpga

Logic Level Modeling Example

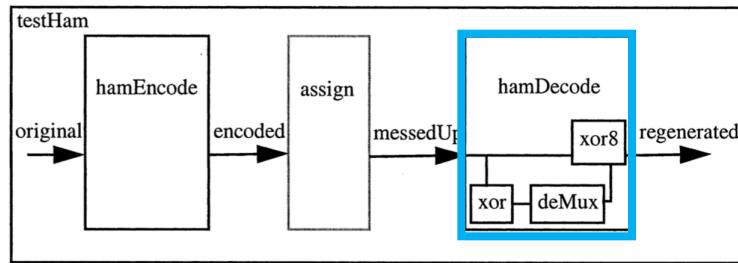

```
module deMux
( output [1:8] outVector,
  input A, B, C, D, enable);
  and v (m12, D, C, ~B, ~A, enable),
    h (m11, D, ~C, B, A, enable),
    d (m10, D, ~C, B, ~A, enable),
    l (m9, D, ~C, ~B, A, enable),
    s (m7, ~D, C, B, A, enable),
    u (m6, ~D, C, B, ~A, enable),
    c (m5, ~D, C, ~B, A, enable),
    ks (m3, ~D, ~C, B, A, enable);

  assign outVector = {m3, m5, m6, m7, m9, m10, m11, m12};

endmodule

module xor8
( output [1:8] xout,
  input [1:8] xin1, xin2
);
  xor a[1:8] (xout, xin1, xin2);

endmodule
```

```
module hamDecode
( input [1:12] vIn,
  output [1:8] valueOut);

  wire c1, c2, c4, c8;

  wire [1:8] bitFlippers;

  xor (c1, vIn[1], vIn[3], vIn[5], vIn[7], vIn[9], vIn[11]),
    (c2, vIn[2], vIn[3], vIn[6], vIn[7], vIn[10], vIn[11]),
    (c4, vIn[4], vIn[5], vIn[6], vIn[7], vIn[12]),
    (c8, vIn[8], vIn[9], vIn[10], vIn[11], vIn[12]);

  deMux mux1 (bitFlippers, c1, c2, c4, c8, 1'b1);

  xor8 x1 (valueOut, bitFlippers, {vIn[3], vIn[5], vIn[6],
    vIn[7], vIn[9], vIn[10], vIn[11], vIn[12]});

endmodule
```



Share:
bit.ly/cloudfpga

Continuous Assignment



- A different way to describe logic is using **assign** continuous assignment statements

```
module oneBitFullAdder
( output cOut, sum,
  input aIn, bIn, cIn
);
  assign sum = aIn ^ bIn ^ cIn,
        cOut = (aIn & bIn) | (bIn & cIn) | (aIn & cIn);
endmodule
```

Boolean algebra-like expression
for each of two assign statements

- Continuous assignment can specify delays

```
module combiningDelays
( input a, b,
  output c
);
  wire #10 c;
  assign #5 c = ~a;
  assign #3 c = ~b;
endmodule
```


Add up delays of
any wires and
assigns when
computing
actual delay

```
module multiplexor
( input a, b, c, d,
  input [1:0] select,
  output e
);
  assign e = mux (a, b, c, d, select);
  function mux
    ( input a, b, c, d,
      input [1:0]select
    );
      case (select)
        2'b00: mux = a;
        2'b01: mux = b;
        2'b10: mux = c;
        2'b11: mux = d;
        default: mux = 'bx;
      endcase
    endfunction
endmodule
```

Functions,
but not tasks,
can be used
in assign
statements

Use default case
to capture
possible x on
the inputs (not
needed for
synthesizable
code, no x)

Continuous Assignment

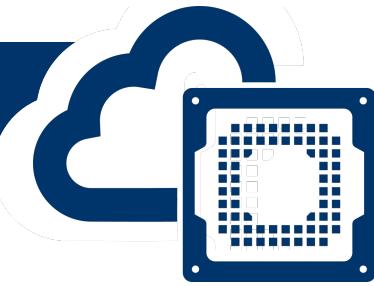

- Continuous assignment can be also used with `inouts` to specify high-impedance output

```
module Memory_64Kx8
( inout [7:0] dataBus,
  input [15:0] addrBus,
  input we, re, clock
);

  reg [7:0] out;
  reg [7:0] Mem [65535:0];

  assign dataBus = (~re) ? out: 16'bz;

  always @(negedge re or addrBus)
    out = Mem[addrBus];

  always @(posedge clock)
    if (we == 0)
      Mem[addrBus] <= dataBus;

endmodule
```


Use `inout` to model a shared data bus where master can drive the bus (writes) or reads the bus (reads)

Assign output to high-impedance when not sending data from memory



Share:
bit.ly/cloudfpga

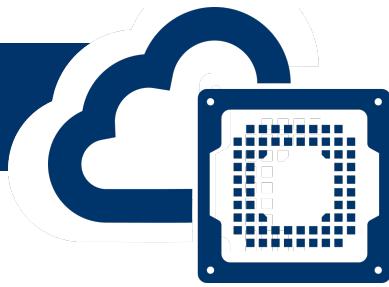Mixing Behavioral and Structural Description



- Most of Verilog code written uses both structural and behavioral descriptions mixed together to describe the design:
 - Use structural for module interconnection, gate-level modeling of certain modules that need specific gate-level implementation
 - Use behavioral for describing modules where specific hardware implementation is less important

Note again, that even with gate-level specification, actual hardware will be different (e.g. using LUTs on FPGAs)

```
module sbus;

parameter Tclock = 20,
          Asize = 5,
          Dsize = 16,
          Msize = 32;

reg clock;
wire rw;
wire [Asize-1:0] addr;
wire [Dsize-1:0] data;

master #(Asize, Dsize) m1 (rw, addr, data, clock);
slave #(Asize, Dsize, Msize) s1 (rw, addr, data, clock);

initial
begin
    clock = 0;
    $monitor ("rw=%d, data=%d, addr=%d at time %d",
              rw, data, addr, $time);
end

always
#Tclock clock = !clock;

endmodule
```


Structural description

Behavioral description



Share:
bit.ly/cloudfpga

Logic Delay Modeling

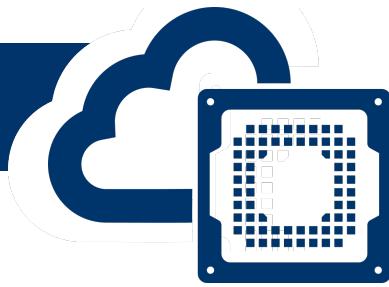

- Gate and net specification can include information about delays
 - Gates can have specified propagation delay for transition to 1, transition to 0, and transition to z, resulting in up to three delay values used with # operator:

(d1 , d2 , d3)


- Delays are used by simulators to determine when to update the values on output of the gates

From value	To value	2 Delays specified	3 Delays specified
0	1	d1	d1
0	x	min(d1, d2)	min(d1, d2, d3)
0	z	min(d1, d2)	d3
1	0	d2	d2
1	x	min(d1, d2)	min(d1, d2, d3)
1	z	min(d1, d2)	d3
x	0	d2	d2
x	1	d1	d1
x	z	min(d1, d2)	d3
z	0	d2	d2
z	1	d1	d1
z	x	min(d1, d2)	min(d1, d2, d3)



Share:
bit.ly/cloudfpga

Minimum, Maximum, and Average Delays

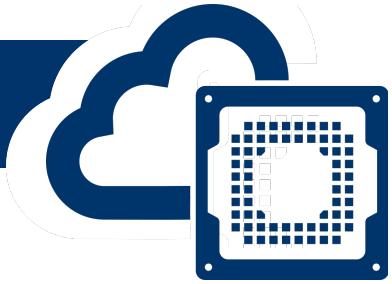

- Verilog allows for three values to be specified for each of the rising, falling, and turn-off delays

- A three-valued delay specification:

```
#(d1, d2, d3)
```

- Can be expanded to:

```
#(dl_min: dl_typ: dl_max, d2_min: d2_typ: d2_max, d3_min: d3_typ, d3_max))
```



Share:
bit.ly/cloudfpga


Logic Delay Modeling



Textbook example of modeling logic gate delays in a tri-state latch:


```
module triStateLatch
( output qOut, nQOut,
  input clock, data, enable
);

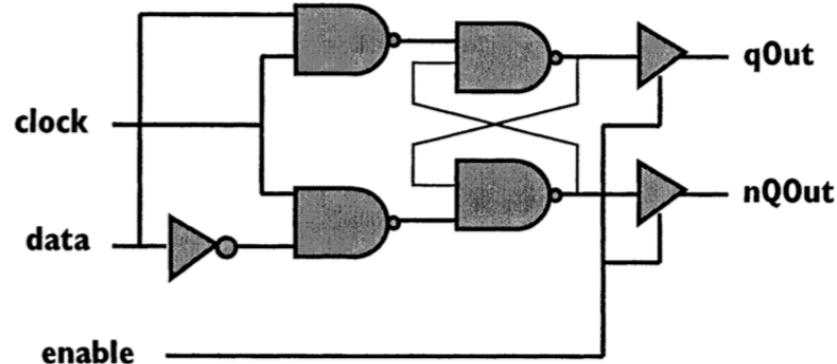  tri qOut, nQOut;
  not #5 (ndata, data);
  nand #(3,5) d(wa, data, clock),
             nd(wb, ndata, clock);
  nand #(12, 15) qQ(q, nq, wa),
                 nQ(nq, q, wb);
  bufif1 #(3, 7, 13) qDrive (qOut, q, enable),
                     nQDrive(nQOut, nq, enable);
endmodule
```



Share:
bit.ly/cloudfpga

Delays Across Modules

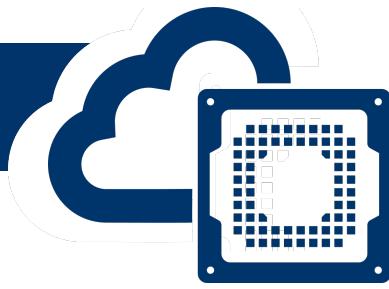

- Verilog allows for modeling delays across a whole module using the **specify** block
 - **source => destination = (delays)** – specifies the delays, same order as for wires: transition to 1, transition to 0
 - **(a, b *> c, d) = (delays)** – combines multiple delay specifications into one: a to c, a to d, b to c, and c to d

```
module dEdgeFF
( input clock, d, clear, preset,
  output q
);


  specify
    specparam tRiseClkQ = 100,
               tFallClkQ = 120,
               tRiseCtlQ = 50,
               tFallCtlQ = 60;

    (clock => q) = (tRiseClkQ, tFallClkQ);
    (clear, preset *> q) = (tRiseCtlQ, tFallCtlQ);
  endspecify
  // Code of the module goes here...
endmodule
```



Share:
bit.ly/cloudfpga

Specifying Time Units

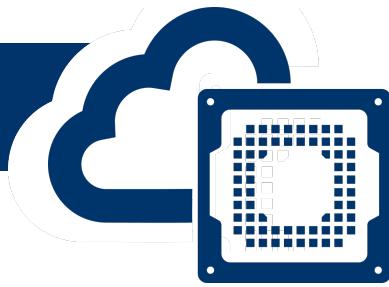

- Verilog simulator works in term of time units, each # delay is in time units
 - To assign specific time unit magnitude to delays use:
``timescale <time_unit> / <time_precision>`
 - Example:
``timescale 10 ns / 1 ns`
- The precision is used to quantify how fine-grained the simulator keeps track of time

Unit of Measurement	Abbreviation
seconds	s
milliseconds	ms
microseconds	us
nanoseconds	ns
picoseconds	ps
femtoseconds	fs

Unit / precision	Delay specification	Time delayed	Comments
10 ns / 1 ns	#7	70 ns	The delay is 7 * time_unit, or 70 ns
10 ns / 1 ns	#7.748	77 ns	7.748 is rounded to one decimal place (due to the difference between 10 ns and 1 ns) and multiplied by the time_unit
10 ns / 100 ps	#7.748	77.5 ns	7.748 is rounded to two decimal places and multiplied by the time_unit
10 ns / 1 ns	#7.5	75	7.5 is rounded to one decimal place and multiplied by 10
10 ns / 10 ns	#7.5	80	7.5 is rounded to the nearest integer (no decimal places) and multiplied by 10



Share:
bit.ly/cloudfpga

References



1. Donald E. Thomas and Philip R. Moorby. "The Verilog Hardware Description Language, Fifth Edition." Springer. 2002



Share:
bit.ly/cloudfpga